


CPE 310 Homework #1: Basic Electronic Circuits

The purpose of this homework is to provide you with practice in simple circuit analysis. *You must show all your work in order to receive full credit.*


Name: _____

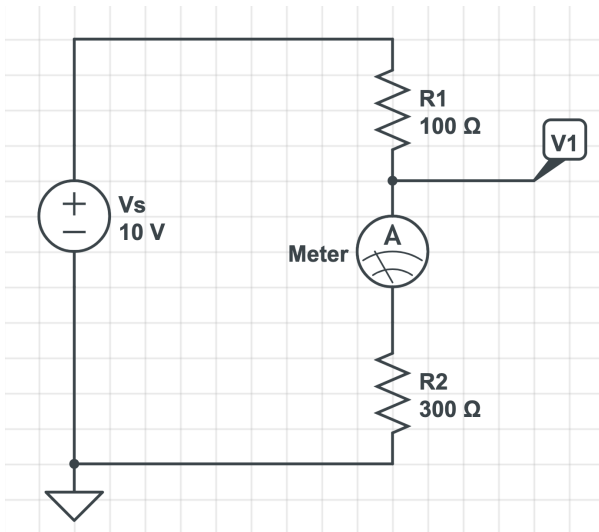I. Series circuit

- Determine the total current through meter A in the circuit shown below.
- Determine the voltage at point V1.




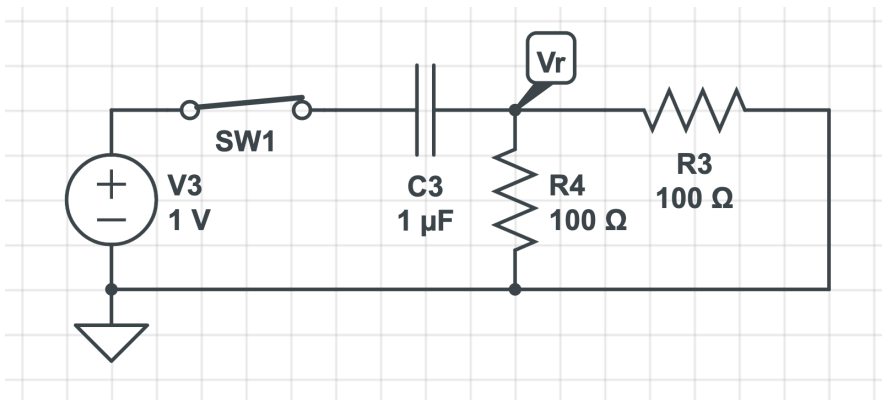- ## II. What is the voltage at point V_r after the switch has been closed for a very long time?




III. Complex resistive circuit

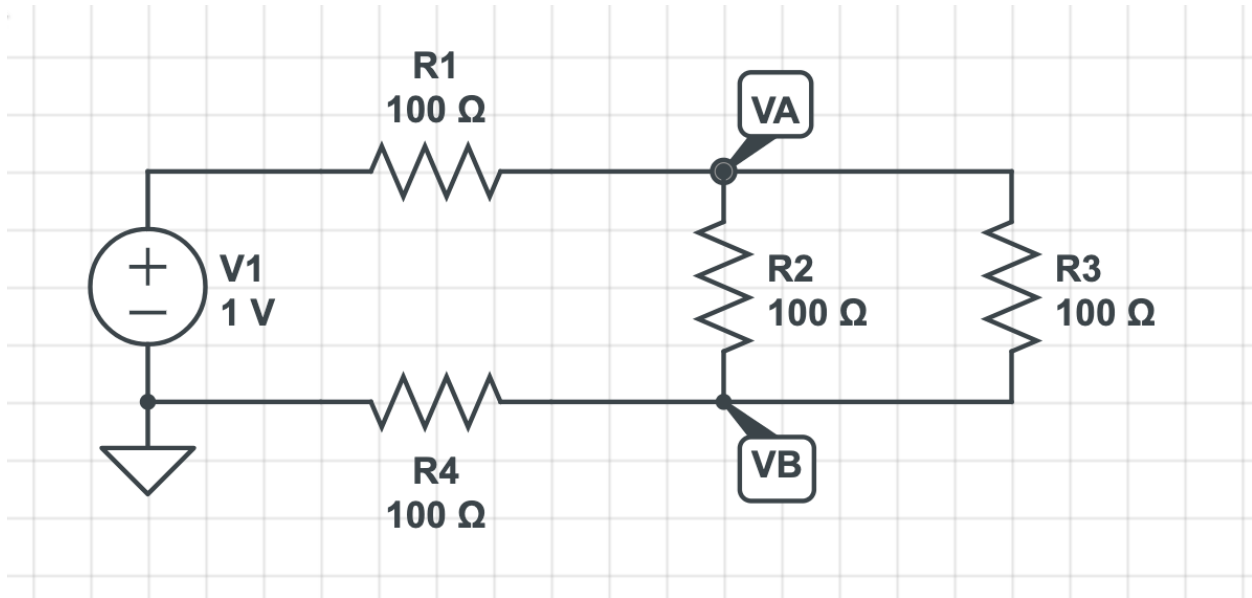- A. What is the total resistance in the circuit? _____
- B. What is the total current in the circuit? _____
- C. Write the Kirchhoff equation for the circuit _____
- D. What is the voltage at point VA? _____
- E. What is the voltage at point VB? _____



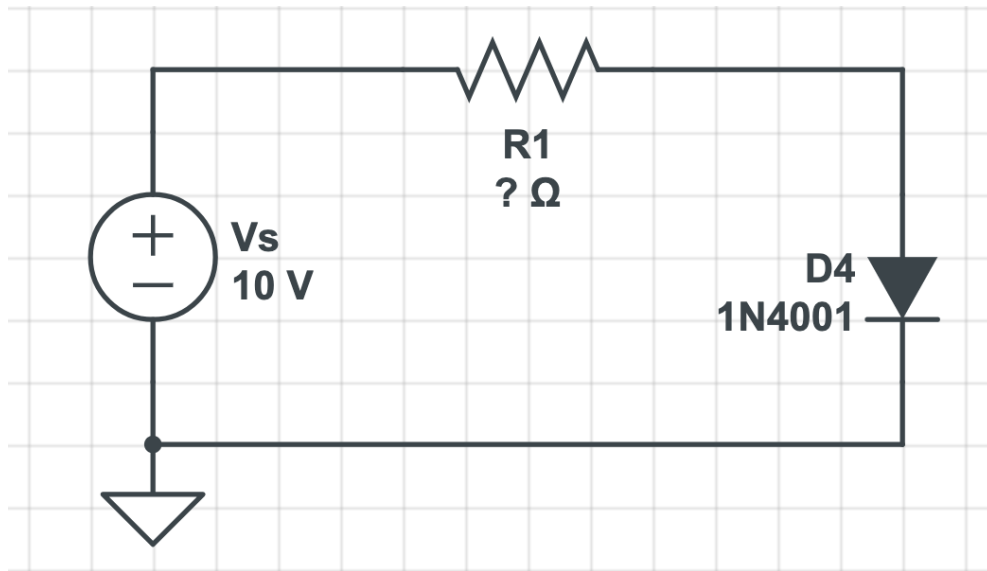- IV. Assume that the diode in the circuit below has a forward bias voltage of 0.7 volts. Calculate the value of resistor needed to cause the current in the circuit / to be 100 mA.



10 Point Bonus

Calculate V_r and V_{out} for the following circuit. Assume the forward bias voltage on D1 is 700 mV as labelled in the diagram.

